

CALIFORNIA STATE UNIVERSITY, FULLERTON
Computer Engineering

EGCP 446 – Advanced Digital Design using Verilog HDL
(Fall 2018)

Midterm Exam 1 (Total Points = 75)

(Time allowed: 7:00 — 9:00 PM)

Academic Dishonesty Policy

In line with University policies, the Computer Engineering program supports a strict and well-defined policy against academic dishonesty. Thus, to assure a fair and equitable testing environment for all students, there will be zero tolerance during exam for any of the following:

- Cheating of any type (looking at or copying another student's answers) or helping another student with answers.
- Use of notes, phones, or other aids (other than that allowed by instructor)
- Talking or texting during exams
- Leaving the classroom during the exam (without permission)


Consequences for violating these policies will be a "zero" on the exam at a minimum, with the possibility of an F in the course.

Only one page of handwritten notes (two side), pens/pencils, erasers, and a calculator (shouldn't be necessary) are allowed with the exam.

Normally, full credit is given only if work is shown when appropriate.

 1. (20 Points) Behavior Modelling

From a 3-bit combinational circuit shown below a) Write the Truth Table b) Express the Boolean functions using either Sum of Products (SOP), or Product of Sums (POS). c) Write a Verilog code to implement the design on an FPGA board.




X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

```
module Comb_Ckt(  
    input X, Y, Z,  
    output F  
);
```

```
endmodule
```

2. (20 Points) Structural Modelling

Verilog code for adder, multiplexer and register is given. Connect all the Verilog modules to create digital circuits shown in the block diagram below.

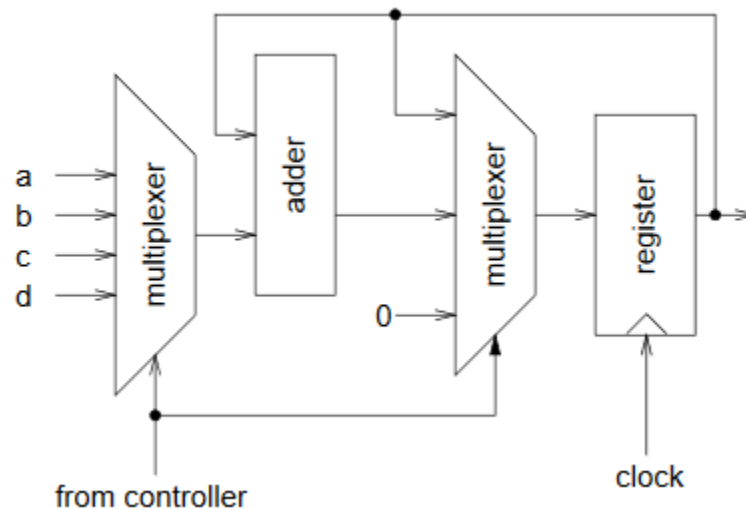**Half Adder**

```
module Half_Adder(
    input A, B,
    output Sum, Carry
);

    assign Sum = A ^ B;
    assign Carry = A & B;
endmodule
```

Multiplexer

```
module Mux(
    input A, B, C, D,
    input [1:0] S,
    output Mux_Out
);

    assign Mux_Out = (S == 0) ? A : (S == 1) ? B : (S == 2) ? C : D;

endmodule
```

Register

```
module Register(
    input D, clock,
    output reg Q
);

    always @ (D, clock)
    if(clock)
        Q <= D ;
endmodule
```

Name: _____

CWID: _____

Date: _____

```
module Top(  
    input a,b,c,d,  
    input [1:0] Ctrl,  
    input Clk,  
    output Sys_out  
);
```

```
endmodule
```

3. (10 Points) RTL Combinational Circuit Design

- a. Draw the schematic for the Verilog code given below;


```
module abc (a, b, c, d, s1, s0);  
    input s1, s0;  
    output a, b, c, d;  
  
    not (s1_, s1), (s0_, s0);  
  
    and (a, s1_, s0_);  
    and (b, s1_, s0);  
    and (c, s1, s0_);  
    and (d, s1, s0);  
  
endmodule
```

- b. Draw the schematic for the Verilog code given below;

```
module Always_Code(  
    input a, b, c,  
    output reg F  
);  
  
always @(a, b, c)  
begin  
    F = ~a | b;  
    F = ~F;  
    F = ~(F & b);  
    F = F & c;  
    F = F | b;  
end  
  
endmodule
```

4. (25 Points) FSM

The following State Diagram is given.

 

a) The state table using D - Flip Flops is shown below. Fill it according to the state diagram.

Present State		Input	Next State		Output
A	B	X	A+	B+	Z

Name: _____

CWID: _____

Date: _____

- b) Write Verilog code to implement the counter (ignore the clock divider)

```
module FSM(  
    input Clk, Reset, X,  
    output Z  
);
```

```
endmodule
```