



CALIFORNIA STATE UNIVERSITY
FULLERTONTM

EGCP 441: Advanced Electronics for Computer Spring 2019

Final Exam Review

Rakesh Mahto, Ph.D.

Office: E 314, California State University, Fullerton

Office Hour: Monday and Wednesday 2:00 - 4:00 pm

Or by appointment

Email: ramahto@fullerton.edu

Phone No: 657-278-7274

Day and Time of Final Exam

- ☐ **Day- May 16, 2019**
- ☐ **Time – 9:30 am – 11:20 am**
- ☐ **Bring pen, pencil, calculator**
- ☐ **One page A4 cheatsheet (both sided)**
- ☐ **Note: Students are not allowed to use phone or computer during the exam.**

Question no 1

☐ Some True and False

- Example: The drain terminal of NMOS is at higher potential than source terminal (True/False)

☐ Fill in the blank

- Example: The drain terminal of NMOS is _____ (higher/lower) potential than source terminal.

Question no 2: Similar to Quiz no 1

Q1. An NMOS transistor is shown in Figure 1. (Use $V_{tn} = 0.5V$, $K_n' = 100 \mu A/V^2$, $W/L = 2$).

Ignore the channel length modulation λ effect. Answer the following questions

- Identify the node names such as drain, gate, source, and body/bulk, based on applied voltage.
- Identify the type of material such as n-type and p-type in the figure below
- If there is an inversion layer then it's consisted of electrons or holes?
- Identify region of operation such as cut-off, linear or saturation? Explain?
- Based on type of region from d) draw the inversion layer under the gate.
- Calculate the current I_D and direction of it.


 


Figure 1 NMOS Transistor

Question no 3: Combination gate

 - Example: A CMOS gate with $V_{DD}=5V$ is designed such that the base $(W/L)=10$. Assume that $V_{Tn}=0.7$, $V_{Tp}=-0.6$, $K'_n=100 \mu A/V^2$, $K'_p=-60 \mu A/V^2$, and the load capacitance is 100fF. Use the constant current source model to find the best case and the worst case t_{pHL} and t_{pLH}



$$OUT = \overline{D + A \cdot (B + C)}$$

Sample question: Voltage Transfer Combination Logic

(30 Points) CMOS Logic Analysis

A three-input CMOS NAND gate is designed as shown below. Assume that $V_{DD}=1.2$ V, $K'_n=90$ $\mu\text{A}/\text{V}^2$, $V_{tn}=0.4$ V, $K'_p=50$ $\mu\text{A}/\text{V}^2$, and $V_{tp}= -0.5$ V in the 100nm technology node.

- (a) Determine the width of NMOS and PMOS transistors in this NAND gate, such that the worst case delay becomes equivalent to a referenced inverter with $W_n=1\mu\text{m}$ and $W_p=2\mu\text{m}$.
- (b) For the device sizes found in part (a), determine the switching threshold voltage, V_M when all inputs are tied together.
- (c) Find the maximum I_{DD} current for this NAND gate.

 



Figure 2 Three input NAND gate

Sample Question no 3: Combination gate

(20 points) Combinational Circuit and Delay Measurement


The following circuit is a dynamic logic.

- What logic function does this perform?
- What input vector imposes the worst case charge sharing during the evaluation time?
- Compute the final voltage at Z, if the input vector is ABCDE=11000 during evaluation after charge sharing. Assume that $V_{th} = 0.4V$.
- Determine the width of the PMOS such that the maximum worst case precharge time delay (0 to 90%) is limited to 250ps. (The worst case is when all the inputs are at V_{DD} such that all the intermediate capacitors contribute to the delay). Assume that $V_{DD} = 1.2V$, $K_p' = 50 \mu A/V^2$, and $V_{th} = -0.5V$ in the 100nm technology node. For simplicity assume that the PMOS will stay in saturation during the transition.

 

 Question no 4: Interconnection Modelling

(40 points) We would like to design the following circuit such that the worst case propagation delays (t_{pHL} and t_{pLH}) are limited to 2.14 ns. Use Elmore delay equation to determine the W/L for PMOS and NMOS used in the 3-input NAND gate. Assume that $V_{DD}=1.2$ V, $K'_n=90 \mu A/V^2$, $V_{tn}=0.4$ V, $K'_p=50 \mu A/V^2$, and $V_{tp}=-0.5$ V in the 100nm technology node. Also assume that the transistors stay in saturation region for the length of the transition.




Sample question no 4: SRAM

EGCP 461 - 02 – Low Power IC Design (Spring 2017)


(20 points) Consider a resistive load SRAM cell schematic shown below, also known as 4 transistor SRAM cell.

 - (a) Assume that node Q is in state 1. In order to write a 0 to node Q, bit line, BL, is lowered to 0 V. Determine the minimal size of transistor M_1 so that the cell just flips when this cell is selected. Assume that the switching threshold V_M of the resistive load inverter equals 0.6V. Also, assume that $V_{DD} = 2.5V$, $R_L = 100K\Omega$, $V_{Tn} = 0.4V$, and $K'_n = 100\mu A/V^2$. Ignore body effect.
- (b) Now assume that node Q is in state 0. In order to read the cell, both bit lines, BL and BL, are pre-charged to V_{DD} . Determine the minimum size of transistor M_2 so that the cell does not flip during a read operation. Assume that $(W/L)_1 = 1.2$, which satisfies the constraint in part (a).






Sample question no 4: Power Calculation

 Q2. [Points 5] Given $V_{DD} = 1.2$ V and $f_{CLK} = 50$ MHz, calculate the activity coefficients and power dissipation at node-D and node-F.



Question no 5: Timing Analysis

- a) Find contamination and critical delay. 
- b) Find the maximum clock frequency for reliable operation. 
- c) The amount of clock skew the circuit can tolerate if it needs to operate at 5 Ghz. 
- d) How much clock skew the circuit can tolerate before it experiences a hold time violation? 